

**DIGITAL LOGIC DESIGN**

(Common to IT and CSE)

Time: 3 hours

Max. Marks: 70

**PART – A**

(Compulsory Question)

\*\*\*\*\*

1 Answer the following: (10 X 02 = 20 Marks)

- If  $1010_2 + 10_2 = X_{10}$ , then X is ----
- Write the first 9 decimal digits in base 3.
- What is meant by don't care condition?
- Why AND and OR are not universal gates? Give the reason.
- Write the truth table of half subtractor.
- Implement AND gate using only two input NOR gates.
- Write the truth table of clocked T-Flip flop.
- Where the ripple counter is used?
- What is the function of EAROM?
- Mention few applications of PAL.

**PART – B**

(Answer all five units, 5 X 10 = 50 Marks)

**UNIT - I**

- Obtain the truth table for the function  $F = xy + xy' + y'z$
  - Prove that the sum of all minterms of a Boolean function for three variables is 1.

OR

- Show that the dual of the exclusive-OR is equal to its complement
  - Convert the decimal number 1973 to base 3, base 5 and base 7.

**UNIT - II**

- Simplify the following Boolean expressions using K-map and implement them using NAND gates:

$$F(W, X, Y, Z) = XZ + WXY + WXY + WYZ + WYZ.$$

OR

- Simplify the following expression using tabulation method:

$$F(A, B, C, D, E) = \sum (4, 6, 7, 9, 11, 12, 13, 14, 15, 20, 22, 25, 27, 28, 30) + d(1, 5, 29, 31).$$

**UNIT - III**

- How full adder is different from full subtractor? Explain.
  - Draw and explain various implementations of full adder.

OR

- What is the function of magnitude comparator? Explain with an example.
  - Design a combinational circuit with four input lines that represent a decimal digit in BCD and four output lines that generate the 9's complement of the input digit.

**UNIT - IV**

- Draw the block diagram of sequential circuit. Explain.
  - What is state assignment? Explain with a suitable example.

OR

- Draw the basic flip flop circuit with NOR gates. Explain its operation.
  - Explain about 3-bit binary counter with a suitable logic diagram.

**UNIT - V**

- Compare PAL and PLA with respect to various performance features.
  - Explain about TTL family.

OR

- Explain about memory decoding error detection and correction.
  - What is the importance of ECL family? Explain.

\*\*\*\*\*