

Code No: 133AJ

R16

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, April/May - 2018

DIGITAL LOGIC DESIGN

(Common to CSE, IT)

Time: 3 Hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART-A**(25 Marks)**

- 1.a) Convert $(67A9)_{16}$ into decimal. [2]
- b) Add (+80) and (-70) using 2's complement. [3]
- c) Write the truth table of Ex-OR Gate. [2]
- d) Implement OR gate using NAND gates only. [3]
- e) Write the truth table of half adder. [2]
- f) Design half subtractor circuit. [3]
- g) Differentiate between Latch and flip flop. [2]
- h) Draw the circuit diagram of Ring counter. [3]
- i) Differentiate between RAM and ROM. [2]
- j) Name any 3 logic micro operations. [3]

PART-B**(50 Marks)**

- 2.a) i) Convert $(657)_8$ into decimal.
 - ii) Convert $(2348)_{10}$ into hexa decimal.
 - b) Represent the decimal number 46.5 as a floating point number with 16 bit mantissa and 8 bit exponent. [5+5]
- OR**
- 3.a) i) Convert 110001.1010010 into hexadecimal.
 - ii) Convert $(423.25)_{10}$ into Hex.
 - b) i) Simplify $A(B+C)+AB+ABC$
 - ii) Write the truth table and symbols of AND and OR gates. [5+5]
4. Obtain the simplified expression in sum of products for the following Boolean function.
 - a) $F(A,B,C,D) = \sum(2,3,12,13,14,15)$.
 - b) $BDE+B'CD+CDE+A'B'CE+A'BC'+B'CD'E'$ [5+5]
- OR**
5. Obtain the simplified expression in product of sums.
 - a) $F(A,B,C,D) = \pi(0,1,2,3,4,10,11)$
 - b) $F(A,B,C,D) = \pi(1,3,5,7,13,15)$ [5+5]

AG AG AG AG AG AG AG A

- 6.a) Design half adder using only NAND gates.
b) Design a combinational circuit which converts BCD to Excess-3 code. [5+5]

OR

- 7.a) Design a 2 bit magnitude comparator.
b) Implement 4*16 decoder using two 3*8 decoders. [5+5]

- 8.a) Explain a right shift register.
b) Design a 3 bit Ripple counter. [5+5]

OR

- 9.a) What is a hazard? How do you eliminate hazards?
b) Design and explain Johnson counter. [5+5]

- 10.a) Explain different types ROMs.
b) Implement the following Boolean functions using PLA with 3 AND gates. [5+5]

$$F_1(ABC) = \sum(3,5,7), \quad F_2 = \sum(4,5,7).$$

OR

- 11.a) Explain the applications of Logic micro operations.
b) Explain shift Right and Left with examples. [5+5]

--0000--

UPIQP.BANK.COM