

R16

Code No: 133BJ

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, November/December - 2017

NETWORK ANALYSIS

(Electronics and Communication Engineering)

Time: 3 Hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART - A

(25 Marks)

- 1.a) Define Graph, Tree, Basic Cut set and Basic Tie set. Illustrate with an example. [2]
- b) Explain Active elements in detail. [3]
- c) Derive the relation between voltage and current in a series connected RL Circuits. [2]
- d) Draw a power triangle in series connected RLC networks. [3]
- e) Derive the relation between RMS and maximum value. [2]
- f) Define form factor and peak factor. [3]
- g) Define characteristic impedance. [2]
- h) Define image and iterative impedance. [3]
- i) Draw and explain T section network. [2]
- j) Explain about LC Filters. [3]

PART-B

(50 Marks)

- 2.a) What is an electric circuit? What is a magnetic circuit? Make a comparison between electric circuit and magnetic circuit.
- b) Coil 1 of a pair of coupled coils has a continuous current of 5A, and the corresponding fluxes ϕ_{11} and ϕ_{12} are 0.2 and 0.4 mWb respectively. If the turns are $N_1 = 500$ and $N_2 = 1500$, find L_1 , L_2 , M and k . [5+5]

OR

- 3.a) For the network shown in below Figure 1 find Z_{ab} and I_o .

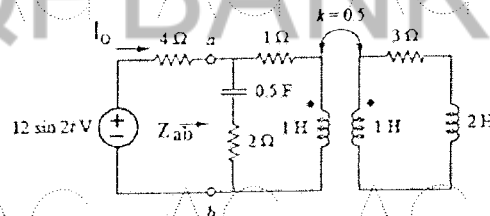


Figure: 1

- b) Find the input impedance of the circuit shown in Figure 2. Assume that the circuit operates at $\omega = 50$ rad/s. [5+5]

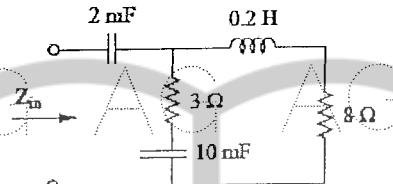


Figure: 2

- 4.a) Obtain the current locus of a fixed resistance and a variable capacitance.
 b) Given a series RLC-circuit with $R = 10$ ohms, $L = 1$ mH and $C = 1$ μ F is connected across a sinusoidal source of 20 V with variable frequency. Find: i) The resonant frequency ii) Q factor of the circuit at resonant frequency iii) Half power frequencies [5+5]

OR

- 5.a) Derive and draw the response of a series RLC circuit for step input.
 b) An impedance $Z_1 = 10 + j10 \Omega$ is connected in parallel with another impedance of resistance 8.5Ω and a variable capacitance connected in series. Find C such that the circuit is in resonance at 5 KHz. [5+5]

6. A series-connected RLC circuit has $R = 4$ and $L = 25$ mH:
 a) Calculate the value of C that will produce a quality factor of 50.
 b) Find ω_1 , ω_2 , and B.
 c) Determine the average power dissipated at $\omega = \omega_0, \omega_1, \omega_2$. Take $V_m = 100$ V. [3+3+4]

OR

- 7.a) Obtain the current locus of a series circuit having a fixed resistance and a variable inductance.
 b) Given a series RLC circuit with $R = 100$ ohms, $L = 0.5$ H and $C = 40$ μ F, Calculate the resonant, lower and upper half – power frequencies. [5+5]

8. Explain clearly the terms:

- a) Characteristic Impedance and
 b) Image Transfer Constant. [5+5]

OR

- 9.a) Define Hybrid parameters of a Two Port network. Establish the relation between Hybrid Parameters and ABCD Parameters.
 b) A symmetrical T-section has an inductance of 0.47H in each series arm and a 300 μ F capacitor in the shunt arm.
 i) Find the characteristic impedance at frequencies of 50 Hz and 100 Hz.
 ii) If the T-section is terminated in the characteristic impedance, find the ratio of load current to input current at both the frequencies. [5+5]

AG AG AG AG AG AG AG A

- 10.a) What is a high pass filter? In what respects it is different from a low pass filter?
b) Derive the equations to find the inductances and capacitances of a constant K high pass filter. [5+5]

OR

- 11.a) What is an LC immittance function? State the properties of such functions.
b) Design a constant 'K' T-section low pass filter having cutoff frequency of 2 kHz and nominal characteristic impedance of 600 ohms. [5+5]

---oo0oo---

AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A