

B.Tech III Year I Semester (R15) Regular Examinations November/December 2017

ELECTRICAL MEASUREMENTS
(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

PART – A
(Compulsory Question)

1 Answer the following: (10 X 02 = 20 Marks)

- State the advantages of PMMC.
- What is a lissajous pattern?
- Write different methods of measurement of medium resistance.
- Define dissipation factor.
- What are the advantages of two wattmeter method?
- What is meant by meter constant of an energy system?
- What is the usual current rating of CT secondary?
- Distinguish between D.C & A.C potentiometers.
- Why are ballistic tests conducted?
- Name any two methods available for the determination of B-H curve of a specimen.

PART – B

(Answer all five units, 5 X 10 = 50 Marks)

UNIT – I

- Derive the torque equation for moving iron instruments.
 - A 2 mA meter with an internal resistance of $100\ \Omega$ is to be converted to 0-150 mA ammeter. Calculate the value of the shunt resistance required.

OR

- Draw the block diagram of CRO & explain briefly the major parts of it.

UNIT – II

- Draw circuit diagram of Wheatstone bridge and derive its balance condition.

OR

- The impedance of the basic a.c bridge are $Z_1 = 50\ \Omega \angle 180^\circ$, $Z_2 = 250\ \Omega \angle 0^\circ$, $Z_3 = 200\ \Omega \angle 30^\circ$. Calculate the constants of unknown impedance.
 - Draw the circuit diagram of Schering bridge and also derive equations under balances.

UNIT – III

- Explain the construction and theory of operation of single phase electro dynamo meter type Wattmeter.

OR

- Derive torque equation of single phase induction type energy meter.

UNIT – IV

- A 250:5, current transformer is used along with an ammeter. If ammeter reading is 2.7A. Estimate the line current.
 - List out differences between C.T & P.T.

OR

- What are the applications of A.C potentiometers?
 - Draw the circuit diagram of D.C Crompton's potentiometer and explain its working.

UNIT – V

- Explain construction and working principle of flux meter with neat sketch.

OR

- How B-H curve is determined using method of reversals?
