

B.Tech III Year I Semester (R15) Regular Examinations November/December 2017

**LINEAR INTEGRATED CIRCUITS & APPLICATIONS**

(Common to ECE and EIE)

Time: 3 hours

Max. Marks: 70

**PART – A**

(Compulsory Question)

\*\*\*\*\*

- 1 Answer the following: (10 X 02 = 20 Marks)
- What is a voltage transfer curve of an Op-amp?
  - List the electrical characteristics of an Ideal Op-amp.
  - Give two reasons why open loop Op-amp is unsuitable for linear applications.
  - Define break frequency & bandwidth.
  - What determines the peak frequency  $f_p$  in the peaking amplifier?
  - Define a filter. How are filters classified?
  - List the important characteristics of basic comparator.
  - Define capture range, lock in range.
  - List the various A/D Conversion techniques & identify the fastest ADC.
  - Describe the various types of SPDT electronic switches used in D/A converter.

**PART – B**

(Answer all five units, 5 X 10 = 50 Marks)

**UNIT – I**

- 2 (a) A dual input unbalanced-output differential amplifier has the following specification:  $|V_{CC}| = 10\text{ V}$ ,  $|V_{EE}| = 10\text{ V}$ ,  $R_{C1} = R_{C2} = 2.7\text{ k}\Omega$ ,  $R_{in} = 50\text{ }\Omega$  and  $R_E = 3.9\text{ k}\Omega$  and the transistor is CA3086 with  $\beta_{ac} = \beta_{dc} = 100$  and  $V_{BE} = 0.715\text{ V}$ . Calculate: (i)  $I_{CQ}$  and  $V_{CEQ}$  values. (ii) Voltage gain. (iii) Input and output resistances.
- (b) Define current mirror circuit. Explain the working of current mirror circuit with necessary equations.

**OR**

- 3 (a) What is an Op-amp? Briefly explain each stages of a typical Op-amp.
- (b) List and explain briefly open loop Op-amp configuration.

**UNIT – II**

- 4 (a) Derive an expression for closed loop voltage gain of an voltage series feedback amplifier for Ideal case.
- (b) Design a compensating network for the LM307 Op-amp. The Op-amp uses  $\pm 10\text{ V}$  supply voltages.

**OR**

- 5 (a) Write the differences between Slew rate and Transient response.
- (b) Write short notes on circuit stability.

**UNIT – III**

- 6 (a) Design a differentiator to differentiate an input signal that varies in frequency from 10 Hz to about 1 KHz. If a sine wave of 1 V peak at 1000 Hz is applied to the differentiator of above part, draw its output waveforms.
- (b) Derive an expression for inverting summing amplifier using three inputs.

**OR**

- 7 What is an instrumentation amplifier? With a neat circuit diagram, explain the working of instrumentation amplifier using Transducer bridge.

Contd. in page 2

## UNIT – IV

- 8 (a) Explain the working of Wein bridge oscillator using Op-amp.  
(b) For Schmitt trigger using Op-amp with  $R_1 = 100 \Omega$ ,  $R_2 = 56 \text{ k}\Omega$ ,  $V_{in} = 1 \text{ Vpp}$  and supply = 15 V. Determine: (i) UTP. (ii) LTP.

OR

- 9 (a) Draw the functional diagram of 555 IC, for astable operation and explain the working.  
(b) Write a short notes on voltage controlled oscillator.

## UNIT – V

- 10 (a) With a neat diagram, explain working of weighted resistor DAC.  
(b) What output voltage would be produced by a DAC controller whose o/p range is 0 to 10 V and whose input binary number is: (i) 0110 (4 bit DAC). (ii) 10111100 (8 bit DAC).

OR

- 11 (a) Explain the working of ADC converter using successive approximation method.  
(b) A dual slope ADC uses a 16 bit counter and a 4 MHz clock rate the maximum input voltage is +10 V. The maximum integration o/p voltage should be -8 V when the counter has cycled through  $2^n$  counts. The capacitor used in the integrator is  $0.1 \mu\text{F}$ . Find the value of the resistor R of the integrator.

\*\*\*\*\*

UPIQPBank.COM