

B.Tech III Year I Semester (R13) Supplementary Examinations November/December 2017

**LINEAR & DIGITAL IC APPLICATIONS**

(Electronics and Instrumentation Engineering)

Time: 3 hours

Max. Marks: 70

**PART – A**  
(Compulsory Question)

\*\*\*\*\*

- 1 Answer the following: (10 X 02 = 20 Marks)
- What is the need for frequency compensation in practical op-amps?
  - List the desirable characteristics of an instrumentation amplifier.
  - What is the need of an op-amp multivibrator?
  - List the applications of IC555 timer in monostable mode of operation.
  - Classify the bipolar logic family by operation and give examples for each category.
  - List some of the differences between CMOS and TTL logic families.
  - List out various steps in an HDL-based design flow.
  - Draw a diagram of the circuit specified by the VHDL code fragment shown below.

```

architecture STR of STRAD is
    component XOR2
    port(X, Y: in BIT; Z: out BIT);
    end component;
    component AND2
    port(L, M: in BIT; N: out BIT);
    end component;
begin
    X1: XOR2 port map (A, B, SUM);
    A1: AND2 port map (A, B, CARRY);
end STR;

```

- Write any two applications of shift registers.
- What is a PLD? Write the classification of PLDs.

**PART – B**

(Answer all five units, 5 X 10 = 50 Marks)

**UNIT – I**



- Design an inverting amplifier with an input resistance of 2 k $\Omega$ , an output resistance of 100  $\Omega$  and an open-circuit voltage gain of -30.
  - List out ideal OP-AMP characteristics.

**OR**

- Design a modified differentiator which has a time constant of 10 ms and a pole frequency of 1 kHz. For a 1 V peak sine-wave input signal at 100 Hz, calculate the peak sine wave output voltage and the relative phase of the output voltage.
  - What are the main features of IC 741 OP-AMP?

  **UNIT – II**


- An operational amplifier is to be used with positive feedback to produce a Schmitt trigger circuit. If resistor,  $R_1 = 10$  k $\Omega$  and resistor,  $R_2 = 90$  k $\Omega$ , what will be the values of the upper and lower switching points of the reference voltage and the width of the hysteresis if the op-amp is connected to a dual  $\pm 10$  V power supply as shown in figure below.



Contd. in page 2

OR

 - 5 (a) Referring to the circuit shown below: (i) Determine the free running frequency  $f_{OUT}$ . (ii) The lock range  $f_L$ . (iii) And the capture range  $f_C$ .



- (b) Write any two applications of 565 PLL with block diagrams.

## UNIT – III

- 6 (a) With the help of function table and circuit diagram explain the CMOS 2-input AND gate.  
(b) With the help of transition time, propagation delay and power dissipation, explain CMOS dynamic electrical behavior.

OR

- 7 Write note on advantages and disadvantages of ECL. Through basic ECL inverter/buffer circuit when input is under HIGH and LOW, explain the principle of an Emitter-Coupled Logic (ECL/CML).

## UNIT – IV

- 8 Explain structural, data flow and behavioral modeling styles of VHDL with suitable examples.

OR

- 9 Write a VHDL program for a prime-number detector using  
(a) Structural modeling style. (b) Process-based dataflow modeling style.

## UNIT – V

- 10 With the help of the truth table, explain the logic diagram of a MSI 74x138 3-to-8 binary decoder and model the same using data flow-style VHDL program.

OR

- 11 What is universal shift register? Draw the truth table, logic diagram of a standard MSI 74x194 4-bit, Universal Shift Register and model the same using data flow-style VHDL program.

\*\*\*\*\*