

B.Tech II Year II Semester (R15) Regular & Supplementary Examinations May/June 2018

ELECTRONIC CIRCUIT ANALYSIS

(Common to ECE & EIE)

Time: 3 hours

Max. Marks: 70

PART – A

(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- Classify feedback amplifiers.
 - Design FET phase shift oscillator for frequency of 2.5 kHz.
 - Write the expression for gain band width product of transmitter amplifier.
 - Show that $g_{b'e} = g_m/h_{fe}$.
 - Three identical cascaded stages have an overall upper 3 dB frequency of 20 KHz and lower 3 dB frequency of 20 Hz. What are the f_L and f_H of each stage?
 - What is the effect of bootstrap technique on emitter follower?
 - The efficiency of transformer coupled class A amplifier expression is _____ and maximum efficiency is _____.
 - Define thermal stabilization and heat sink.
 - Define Q-factor of a small signal tuned amplifier with relevant expression.
 - When single tuned amplifier is cascaded? What is the effect on bandwidth of the cascaded amplifier?

PART – B

(Answer all five units, 5 X 10 = 50 Marks)

UNIT – I

- 2 (a) Explain the characteristics of the negative feedback amplifier.
 (b) The closed loop gain of a (-ve) feedback amplifier is measured as 99.7 when feedback factor is 1/100 and as 297 when a feedback factor of 1/300 is used. Determine open loop gain.

OR

- 3 (a) Explain the operation of Hartley oscillator using FET amplifier.
 (b) Design a phase shift oscillator to have 3 kHz cutoff frequency use a single stage BJT amplifier with power supply = $\pm 15V$ and $\beta \geq 100$.

UNIT – II

- 4 Derive an expression for CE short circuit current gain.

OR

- 5 Derive an expression for voltage gain, input and output impedance of common source FET amplifier.

UNIT – III

- 6 Derive an equation for voltage gain, current gain, input impedance and output impedance of Darlington emitter follower.

OR

- 7 Illustrate two stage transistor amplifier with neat circuit diagram and relevant expressions.

UNIT – IV

- 8 Define second harmonic distortion. Derive an expression for second harmonic component of transmitter amplifier.

OR

- 9 (a) Briefly explain MOSFET power amplifier.
 (b) Define cross over distortion and explain the operation of class AB power amplifier.

UNIT – V

- 10 Describe the operation of single tuned amplifier with neat circuit diagram and relevant expression.

OR

- 11 Illustrate the operation of double tuned amplifier with neat circuit diagram and necessary equation.
