

Code No: 133AB

R16

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, November/December - 2018

**ANALOG ELECTRONICS**  
(Common to ECE, ETM)

Time: 3 Hours

Max. Marks: 75

**Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

**PART- A**

(25 Marks)

- 1.a) What are the types of distortion in amplifiers. [2]
- b) Classify the amplifiers according to the method of coupling. [3]
- c) Why the h parameter model is not suitable to analyze transistor at high frequencies. [2]
- d) What are the elements in the Hybrid 'II' model? [3]
- e) What is cascode amplifier? [2]
- f) State the advantages and disadvantages of the source follower. [3]
- g) What is meant by positive and negative feedback? [2]
- h) State the Barkhausen criterion for oscillations. [3]
- i) What are the requirements of a tuned amplifier? [2]
- j) Give the definition of power amplifier. Also list the types in it based on location of Q point. [3]

**PART-B**

(50 Marks)

2. Draw the h-parameter equivalent circuit for a typical common emitter amplifier and derive expression for  $A_i$ ,  $A_v$ ,  $R_i$  and  $R_o$ . [10]
- OR
3. Draw simplified h parameter equivalent circuit and calculate  $A_i$ ,  $A_v$ ,  $A_{v_s}$ ,  $R_i'$  and  $R_o'$  for the cascode circuit shown in figure 1. Assume that transistors are identical with  $h_{fe}=10$ ,  $h_{ie}=2\text{ K}\Omega$ ,  $h_{re}=h_{oe}=0$ . [10]

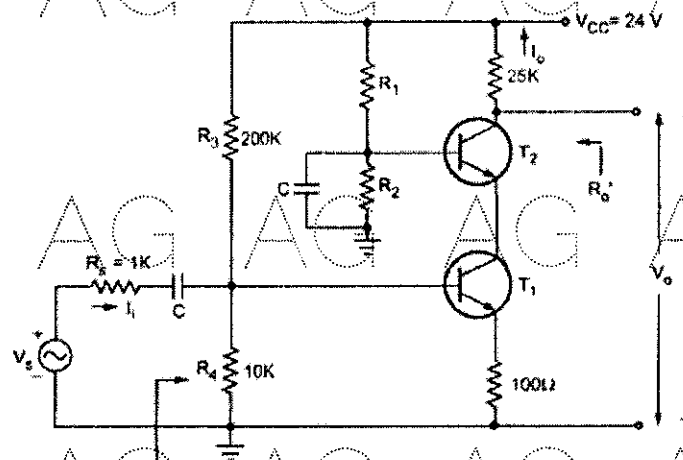


Figure: 1

- 4.a) Derive an expression for current gain with resistive load.  
 b) The hybrid-  $\Pi$  parameters of the transistor used in the circuit shown in figure 2 are  $g_m = 50 \text{ mA/V}$ ,  $r_{b'e} = 1 \text{ K}\Omega$ ,  $r_{b'c} = 4 \text{ M}\Omega$ ,  $r_{ce} = 80 \text{ K}\Omega$ ,  $C_c = 3 \text{ pF}$ ,  $C_e = 100 \text{ pF}$  and  $r_{bb} = 100 \Omega$ , find (i) upper 3 dB frequency of current gain (ii) the Magnitude of voltage gain at  $A_{vs} = V_o/V_s$  at frequency of part (i) [5+5]

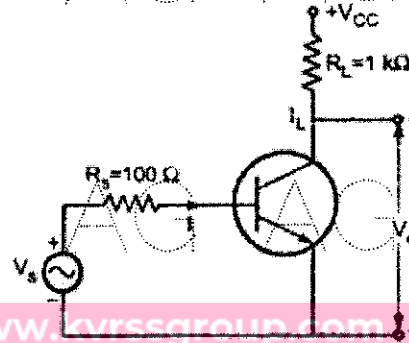


Figure: 2  
OR

- 5.a) A single stage CE amplifier is measured to have a voltage gain bandwidth  $f_H$  of 5 MHz with  $R_L = 500 \Omega$ . Assume  $h_{fe} = 100$ ,  $g_m = 100 \text{ mA/V}$ ,  $r_{bb} = 100 \Omega$ ,  $C_c = 1 \text{ pF}$  and  $f_T = 400 \text{ MHz}$ . (i) find the value of source resistance that will give the required bandwidth. (ii) with the value of  $R_s$  found in (i), find the mid band voltage gain  $V_o/V_s$ .  
 b) In hybrid 'pi' model of a transistor at high frequencies, show that the  $g_m$  is proportional to the collector current. [5+5]
- 6.a) Discuss the input and output characteristics of a folded cascade amplifier with NMOS input.  
 b) Derive expression for  $A_v$  and  $R_o$  for common gate amplifier. [5+5]
- OR
- 7.a) Draw and explain the CS stage with diode connected load.  
 b) Discuss the MOSFET characteristics in depletion mode. [5+5]
- 8.a) Show that for a current series feedback amplifier the input and output resistances are increased by a factor of  $(1+A\beta)$  with feedback.  
 b) Identify the topology of feedback in the circuit of figure 3 giving Justification. Two transistors are identical with  $h_{ie} = 2 \text{ K}$  and  $h_{fe} = 100$ . Calculate i)  $R_{if}$  (ii)  $A_{if}$  (iii)  $A_{vf}$  [5+5]

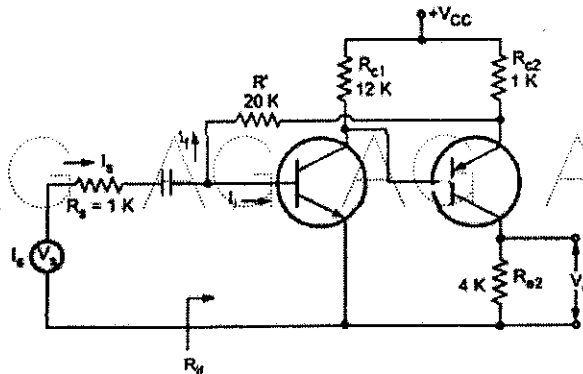


Figure: 3  
OR

9.a) Explain the principle of operation of the wein bridge oscillator.

b) Mention the features and advantages of the crystal oscillator.

[5+5]

10.a) Show that the transformer coupled class A amplifier maximum efficiency is 50%.

b) Compare the push-pull class B and complementary symmetry class B amplifier.

[5+5]

OR

11.a) A tuned amplifier is required to have a voltage gain of 30 at 10.7 MHz with 200 KHz BW. An FET with  $g_m=5 \text{ mA/V}$  and  $r_d=100 \text{ K}\Omega$  is available. Calculate the values of tank circuit elements.

b) Draw and explain the frequency response of tuned amplifier.

[5+5]

---oo00o---

