

R16

Code No: 133AJ

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, November/December - 2018

DIGITAL LOGIC DESIGN

(Common to CSE, IT)

Time: 3 Hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART - A

(25 Marks)

- 1.a) Write the advantages of floating-point representation. [2]
- b) Distinguish between weighted and non-weighted codes with example. [3]
- c) What is the use of don't care combinations? [2]
- d) Implement the following function using only NOR Gates $F = a.(b + c) + (b.c)$. [3]
- e) Define a combinational circuit, give its block diagram. [2]
- f) Write a short notes on priority encoder. [3]
- g) Differentiate between a latch and a flip flop. [2]
- h) Define Hazard. Mention various types of hazards. [3]
- i) Why programmable AND gates are used in PLA instead of a decoder. [2]
- j) Write the applications of logical micro operations. [3]

PART-B

(50 Marks)

- 2.a) Implement AND, OR, NOR by using NAND gates only.
- b) Derive the hamming code for the sequence (101011). [5+5]

OR

- 3.a) Convert the following to the corresponding bases
 - i) $(343)_5 = (\quad)_6$
 - ii) $(7654)_8 = (\quad)_{10}$
- b) Explain about even and odd parity check with an example, what is the drawback. [5+5]

- 4.a) Derive the sum of minterms for $f(a,b,c,d) = a'b + ab'd + c'd$
- b) Derive and Implement Exclusive OR function involving three variables using only NAND function. [5+5]

OR

- 5.a) Obtain the simplified expression in POS (product of sums) of $F(w,x,y,z) = \pi(1,2,4,7,12,14,15)$ using K-maps.
- b) Implement the function $f(a,b,c) = \sum(1,3,4,6)$ using NOR-NOR two level gate structure. [5+5]

6. Realize a full subtractor using decoders. [10]

OR

- 7.a) Define a multiplexer? Draw a 2:1 multiplexer for the function $f(x,y,z) = \sum(0,2,3,5,7)$
- b) Write the steps involved in designing a combinational circuit. [5+5]

8. What is the drawback of JK flip flop, design a flip flop which overcomes this drawback and explain with neat diagram. [10]

OR

- 9.a) Draw the block diagram of asynchronous sequential circuit.
b) Analyze latch with NOR gates, derive transition, flow and state tables. [4+6]

10. Give the logic implementation of a 32×4 bit ROM using decoder of a suitable size. [10]

OR

11. What do you mean by register transfer? Explain in detail. Also discuss Three state bus buffer. [10]

---oo0oo---

