

Code No: 133BK

**R16**

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**

**B.Tech II Year I Semester Examinations, November/December - 2018**

**NETWORK THEORY**  
(Electrical and Electronics Engineering)

**Time: 3 Hours**

**Max. Marks: 75**

**Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.


Each question carries 10 marks and may have a, b, c as sub questions.

**PART- A**

- (25 Marks)
- What is cut set matrix? [2]
  - Define: i) Flux ii) Reluctance iii) M.M.F. [3]
  - What is balanced supply and balanced load? [2]
  - What is the significance of phase sequence? [3]
  - Sketch the DC response of RL circuit and response curve. [2]
  - Define time constant of R-C circuit excited d.c source. [3]
  - Define Port and Two-port network. [2]
  - Two two-port networks with transmission parameters  $A_1, B_1, C_1, D_1$  and  $A_2, B_2, C_2, D_2$  respectively are cascaded. What is the transmission parameter matrix of the cascaded network? [3]
  - What is the function of a band elimination filter? [2]
  - What is a high pass filter? In what respects it is different from a low pass filter? [3]

**PART-B**

- (50 Marks)
- Explain self inductance and mutual inductance.
  - Find the value of XL in the coupled network shown in figure 1 for making it series resonant. [5+5]

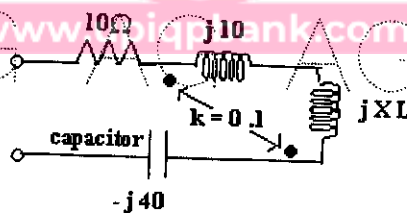

**Figure: 1**  
**OR**

- 3.a) Obtain tie-set schedule for the network shown in figure 2.

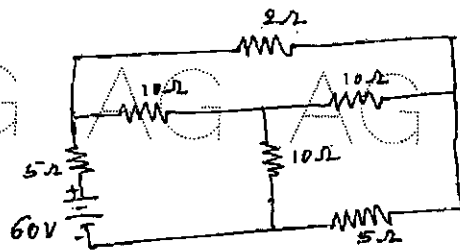


Figure: 2

- b) Explain Faradays law of electromagnetic Induction.

[5+5]

- 4.a) An unbalanced  $\Delta$  connected load is connected across a balanced 3 phase RYB 440V supply. Find the wattmeter reading connected in the circuit shown in figure 3.

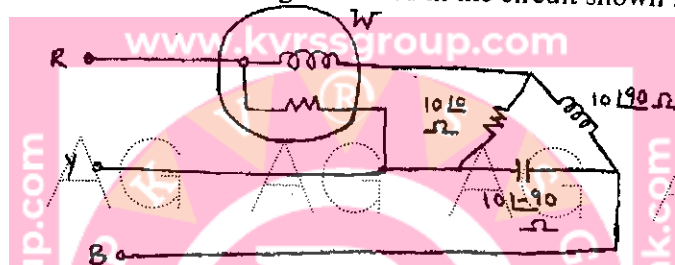


Figure: 3

- b) Three impedances  $Z_a = 6\angle 90^\circ$ ,  $Z_b = 6\angle 0^\circ$  and  $Z_c = 6\angle -90^\circ$  ohms are connected in star. Calculate the values of  $Z_x$ ,  $Z_y$  and  $Z_z$  of the equivalent delta. Derive the formula used.

[5+5]

OR

5. A balanced three phase three wire system has a Y-connected load. Each phase contains three loads in parallel:  $-j 100 \Omega$ ,  $100 \Omega$  and  $50 + j50 \Omega$ . Assume positive phase sequence with  $V_{ab} = 400\angle 0^\circ$  volts. Find (i)  $V_{an}$  (ii)  $I_{aA}$  (iii) The power factor of the load (iv) The total power drawn by the load.

[10]

- 6.a) The switch in Figure 4 has been in position A for a long time. At  $t=0$ , the switch moves to B. Determine  $v(t)$  for  $t > 0$  and calculate its value at  $t=1$  s and 4 s.

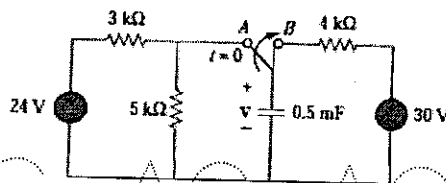


Figure: 4

- b) Find the Capacitor voltage for  $t < 0$  and  $t > 0$  for each circuit shown figure 5.

[5+5]

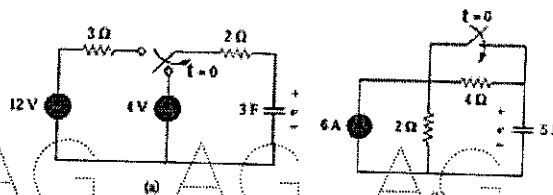


Figure: 5

- OR
- 7.a) At  $t = 0$ , switch 1 in Figure 6 is closed, and switch 2 is closed 4 s later. Find  $i(t)$  for  $t > 0$ . Calculate  $i$  for  $t = 2$  s and  $t = 5$  s.

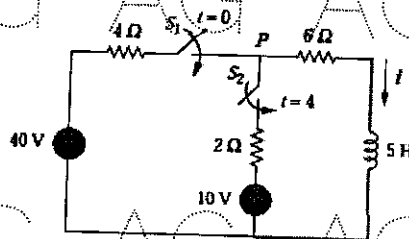


Figure: 6

- b) The switch has been in position a for a long time as shown in figure 7, At  $t=0$  it moves to position b. Calculate  $i(t)$  for all  $t > 0$ . [5+5]



Figure: 7

- 8.a) Explain different types network functions as applied to single port and two port network. Obtain  $Y_{12}$  of the given network shown in figure 8.

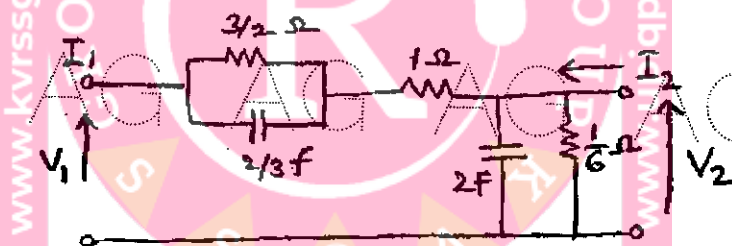


Figure: 8

- b) Obtain the relation between Y and Z parameters. [5+5]
- OR
- 9.a) Find driving point impedances  $Z_{11}$  and  $Z_{22}$  transfer impedances  $Z_{21}$  and  $Z_{12}$  for the network shown in figure 9.

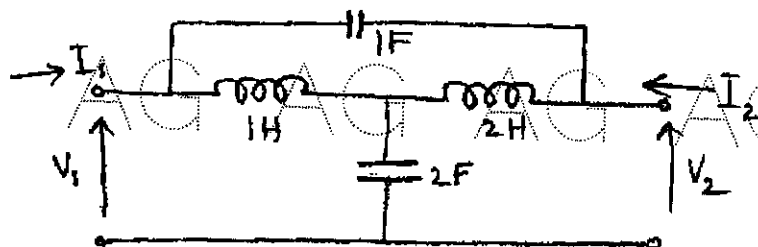


Figure: 9

- b) Obtain the relationship between Z and h parameters. [5+5]

10. Derive the equations to find the inductances and capacitances of a constant K high pass filter. [10]

OR

11. Explain low pass filters. Discuss the design considerations of K type-low pass filters. [10]

—oo0oo—

