

II B. Tech I Semester Supplementary Examinations, May - 2019
BASIC ELECTRICAL AND ELECTRONICS ENGINEERING
 (Com to CE & PE)

Time: 3 hours

Max. Marks: 70


- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answer **ALL** the question in **Part-A**
 3. Answer any **FOUR** Questions from **Part-B**

PART -A

1. a) State Kirchoff's Laws. (2M)
- b) What is the function of starter in a dc motor. (3M)
- c) List out different types of losses that occur in the core of a transformer. (3M)
- d) A 6 pole, 3 phase induction motor is supplied from 50 Hz. Determine its synchronous speed. (2M)
- e) Explain briefly about PN junction diode. (2M)
- f) What is PNP junction transistor? (2M)

PART -B

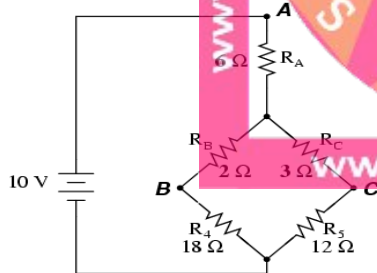2. a) Explain in detail about series and parallel combination of resistances, inductances and capacitances. (7M)
- b) Find voltage across 12Ω resistance in the below figure. (7M)



3. a) Derive emf equation of a dc machine (7M)
- b) Explain in detail about principle of operation of dc motor. (7M)
4. a) Discuss the constructional features and operation of a transformer (7M)
- b) A kVA, 200/500 V, 50 Hz, single phase transformer has equivalent resistance referred to primary is 0.15Ω . Find total copper losses on full load and efficiency while supplying full load at 0.9 p.f. lagging. (7M)

5. a) Draw and explain torque-slip characteristics of a induction motor. (7M)
- b) A 3-phase, 12 pole alternator is coupled to an engine running at 500 rpm. the alternator supplies an induction motor which has a full load speed of 155 rpm. Find the slip and number of poles of the motor. (7M)
6. a) Discuss in detail about half wave rectifier. (7M)
- b) Explain in detail about full bridge rectifier. (7M)
7. a) Discuss briefly about single stage CE Amplifier. (7M)
- b) Describe clearly about frequency response of CE amplifier. (7M)

